OBSERVATORY SCIENCE AND TECHNOLOGY (ST) Teacher's Guide A Second Year of Secondary Cycle Two

HOW DOES IT WORK?

STUDENT LOG

WORKING DOCUMENTS

The case study	1
Creating the context	3
Gathering information	7
Completing the case study	16
Validating the case study	18
EVALUATION DOCUMENTS	
My evaluation	20
Evaluation grid	21

PROCEDURE AND EVALUATION: SSC2 – TECHNOLOGY



LES 12



The case study

One winter evening there's a power outage.

After groping around and finally finding your flashlight, you realize that the batteries are flat. But there are no more batteries in the house.

Why not buy a BATTERY-FREE FLASHLIGHT for the next time?

Our flashlight model works with a **dynamo**, a device that converts mechanical energy into electrical energy through electromagnetic induction. All you have to do is turn the handle a few times to recharge the **storage battery** (a 3.6-V Ni-MH lithium battery).

EFFICIENT

No more incandescent bulbs, which transform only 5 percent of all the electrical energy they consume into light energy and lose 95 percent in heat. Our flashlight is equipped with three LEDs (light-emitting diodes), which are energy-efficient electronic components that emit light when current flows through them.

POWERFUL

With the white light from the three LEDs, you can see more than 10 m in front of you.

ECONOMICAL

The battery can be recharged at least **500 times**. In theory, if you use our dynamo flashlight once a week, it should last at least **10 years**.

PRACTICAL

Compact and light, our flashlight is always ready to use, whether you're camping, travelling or caught in an emergency (power outage, car breakdown).

ENVIRONMENTALLY FRIENDLY

No batteries to buy or throw away. Using this dynamo flashlight helps protect the environment.

Turning the handle for 1 minute \approx 10 minutes of light

Observatory / Guide 11129-A



ST

The case study (continued)

PROPOSAL FOR RESEARCH ON FLASHLIGHTS

Dynamo flashlights are becoming more widely available on the market. Before deciding whether to recommend them, we would like to conduct a study to compare the energy consumption of this type of flashlight (with a dynamo and LEDs) to the energy consumption of a traditional flashlight (with batteries and incandescent bulbs).

First, we will analyze the technology behind a dynamo flashlight. Then, we will pursue the analysis by measuring the following data in model electrical circuits of the two types of flashlights:

- the potential difference of the power supply
- the potential difference at the terminals of each circuit element
- the total current intensity
- the current intensity flowing through each of the circuit elements

We will thus be able to calculate the value of each of the resistors in the circuit, the energy consumed by each flashlight after 10 minutes' use and the energy consumed by each LED or bulb.

Centre for Environmental Studies

In this context, you will play the role of an expert who must issue a recommendation for or against the purchase of dynamo flashlights.



Creating the context

I ask myself questions

- 1. What is a flashlight?
- 2. What is a dynamo?

3. What is an LED?

- 4. What is an incandescent bulb?
- **ERPI** Reproduction and adaptation permitted solely for classroom use with *Observatory*.

5. What is an electrical circuit?

6. What is a circuit diagram?

Observatory / Guide 11129-A



 \rangle

ST

Creating the context (continued)

7. What questions should guide you in your technological analysis of the dynamo flashlight and in your information gathering?

I must

8. Reformulate the goal of the case study.



Creating the context (continued)

I think

9. Would you recommend the purchase of a dynamo flashlight? Explain your answer.

What I know and what I must find out

10. Write the information you already know and the information you need to find out.

What I know

What I must find out



5

Creating the context (continued)

I prepare

11. Where will you find the information you need to do your work?

12. Define the main steps of your case study in chronological order.

Reflection	Yes	No
Do I fully understand what I have to do?		



Gathering information

I do research

1. What is electrical charge? What is its unit of measurement?

2. What is the difference between static electricity and dynamic electricity?

- 3. What is electric current?
- 4. What is current intensity? What is its unit of measurement?

5. What is the mathematical formula for the relationship between current intensity and electrical charge? Identify each variable and its unit of measurement.



6. What is potential difference? What is its unit of measurement? 7. What is the formula for the relationship between potential difference and electrical charge? Identify each variable and its unit of measurement. 8. What is electrical resistance? What is its unit of measurement? 9. What is Ohm's law? Write the mathematical formula that describes the law and identify each variable and its unit of measurement. 10. How is a value of electrical resistance determined?

ST



ST

Gathering information (continued)

11. Briefly explain what you should do to collect the data you need to calculate the resistance value of each of the resistors in the flashlight circuits.

12. What is electrical power?

13. What is the mathematical formula for calculating electrical power in this case study? Identify each variable and its unit of measurement.

14. What is the mathematical formula for calculating electrical energy? Identify each variable and its unit of measurement.



15. a)	What is a series circuit?
b)	What is a parallel circuit?
16. a)	What is a magnetic field?
b)	How can the presence of a magnetic field be detected? Explain your answer.
c)	What can generate a magnetic field?

0

____ ____



I analyze my results

17. What is the general purpose of a dynamo flashlight?

18. Suggest some constraints (material, human or aesthetic) that may have guided the design of the dynamo flashlight.

19. a) What does the dynamo do?

b) What do the gears do?

20. Are light-emitting diodes connected in series or in parallel? Explain your answer.

21. Are light-emitting diodes connected in series or in parallel with their resistors? Explain your answer.

Observatory / Guide 11129-A



22. Draw the circuit diagram of the dynamo flashlight and give your diagram a title. In the diagram, identify the points at which you will take the various readings, the devices you will use and how they will be connected.



- **23.** a) Have your dynamo flashlight circuit diagram approved.
 - **b)** In the space below, prepare a table for recording your results and measurements. Remember to give it a title.
 - c) Complete the table with your measurements.



ST

Gathering information (continued)

24. Draw the circuit diagram of the traditional flashlight and give your diagram a title. In the diagram, identify the points at which you will take the various readings, the devices you will use and how they will be connected.



- **25.** a) Have your traditional flashlight circuit diagram approved.
 - b) In the space below, prepare a table for recording your results and measurements. Remember to give it a title.
 - c) Complete the table with your measurements.

Reflection	Yes	No
Do I fully understand the concepts covered in this situation?		



Completing the case study

1. Calculate the resistance of each of the circuit components in the dynamo flashlight.

2. Calculate the energy consumed by each of the LEDs in 10 minutes.

3. Calculate the energy consumed by the dynamo flashlight circuit in 10 minutes.

Completing the case study (continued)

4. Calculate the resistance of each of the circuit components in the traditional flashlight.

5. Calculate the energy consumed by each of the bulbs in 10 minutes.

6. Calculate the energy consumed by the traditional flashlight circuit in 10 minutes.

Reflection

Yes No

Have I considered other approaches?

Observatory / Guide 11129-A



Validating the case study

I justify my approach

- 1. Case study conclusions:
 - a) Would you recommend the purchase of a dynamo flashlight? Justify your answer, taking into consideration the calculations you have done and the environmental impact of each of the flashlights.



0

_ 🗖



Validating the case study (continued)

b) Are there any other factors to take into account before advising for or against the purchase of dynamo flashlights?

2. Suggest improvements to your work.



My evaluation

Name:

Use the evaluation of the following page to evaluate yourself. Write A, B, C, D or E in the "Me" column of the chart below.

SS	C2—Makes the most of h	is/h	er kno	owledge of science and technology
Criteria*	Observable indicators	Me	Teacher	Comments
1	Creating the context			
	Definition of the goal and description of the procedure			
			With help	
2	Gathering information			
	Completion of the circuit diagrams and collection of relevant data			
	and collection of relevant data			
			□ With	
			help	
3	Completing the case study			
	Calculations			
			□ With	
			help	
4	Validating the case study			
	Justification of the recommendation			
			□ With	
			help	

* Evaluation criteria

- **1** Formulation of appropriate questions
- 2 Appropriate use of scientific and technological concepts, laws, models and theories
- 3 Relevant explanations or solutions
- 4 Suitable justification of explanations, solutions, decisions or opinions



$\mathbf{>}$	*Criteria	٢
-		-
Observatory / Guid 11129-	le A	

igsilon SSC2 $_{-1}$ Makes the most of his/her knowledge of science and technology

siretia	Observable indicators	A	B	υ	D	ш
1	Creating the context	The goal of the case study is very clearly	The goal of the case study is clearly defined	The goal of the case study is not very clearly	The goal of the case study is not very clearly	The work must be
	Definition of the goal and description of the procedure	defined, and all of the steps in the procedure are relevant.	and most of the steps in the procedure are relevant.	defined, OR some of the steps in the procedure are irrelevant.	defined. AND some of the steps in the procedure are irrelevant.	done again.
2	Gathering information	The circuit diagrams are well-drawn	The circuit diagrams represent the flashlight	The circuit diagrams contain many errors, OR	The circuit diagrams contain many errors, AND	The work must be
	Completion of the circuit diagrams and collection of relevant data	representations of the flashlight circuits. All the relevant data has been collected and recorded properly.	circuits, but they contain minor errors. Most of the relevant data has been collected and recorded properly.	only some of the relevant data has been collected and recorded properly.	only some of the relevant data has been collected and recorded properly.	done again.
e	Completing the case study	The required calcula- tions are complete and	The required calcula- tions are complete. but	The calculations contain many errors or are	Most of the calculations are incorrect or irrelevant.	The work must be
	Calculations	correct. All the units of measurement are indicated correctly.	they contain minor errors.	irrelevant.		done again.
4	Validating the case study	The justification is relevant and very clear.	The justification is relevant and clear.	The justification is partially relevant.	The justification is not very relevant.	The work must be
	Justification of the recommendation					done again.

LES12

Evaluation criteria

1 Formulation of appropriate questions

2 Appropriate use of scientific and technological concepts, laws, models and theories

3 Relevant explanations or solutions

4 Suitable justification of explanations, solutions, decisions or opinions

Evaluation grid